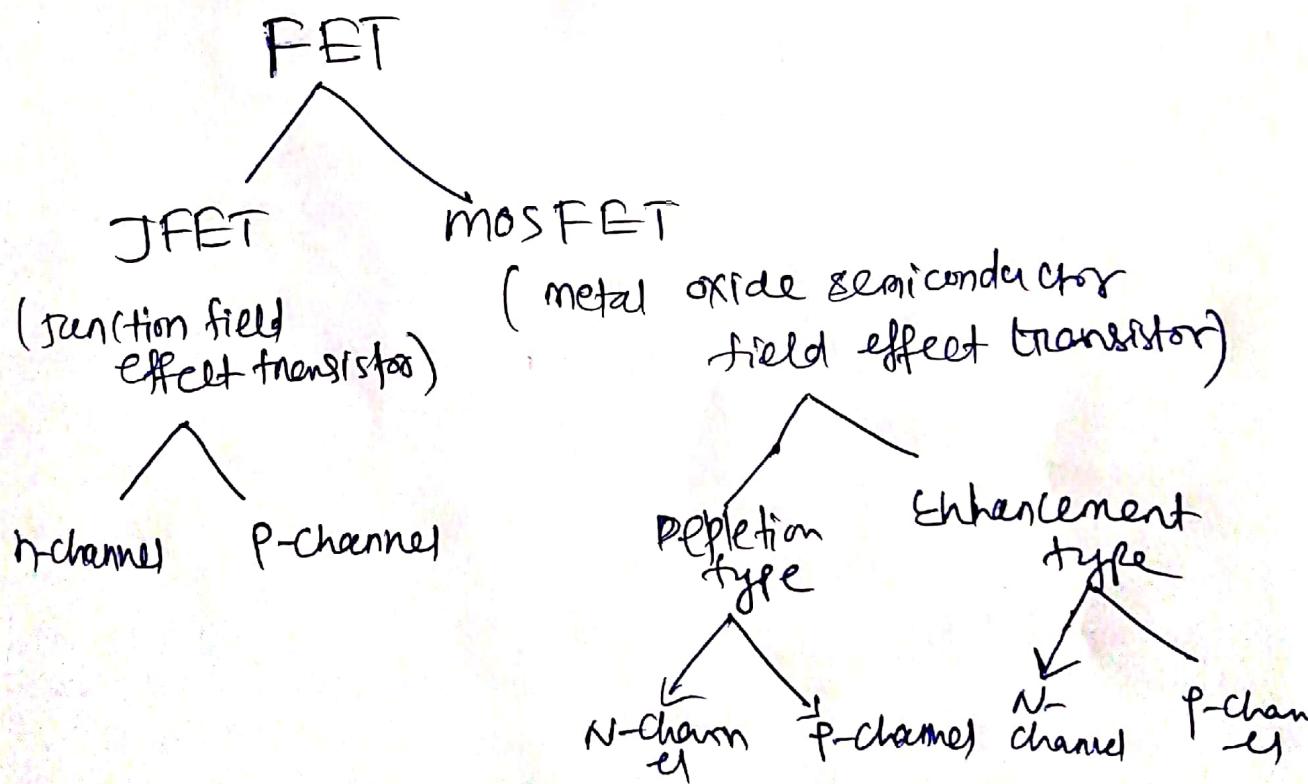


Field effect transistor

- * classification of FET
- * Advantages of FET over BJT
- * principle of operation of BJT
- * FET parameters
 - * DC drain resistance
 - * AC drain " "
 - * Trans-conductance

* Classification of FET :



FET



It stands for field effect transistor
Three terminals are source/gate, drain
It is unipolar device as current flows due to electron flow.

It is a voltage control device, gate voltage controls current and low op resistance
high input resistance


- * less noisy
- * high efficiency
- * longer life
- * switching speed high
- * small gain bandwidth product

BJT

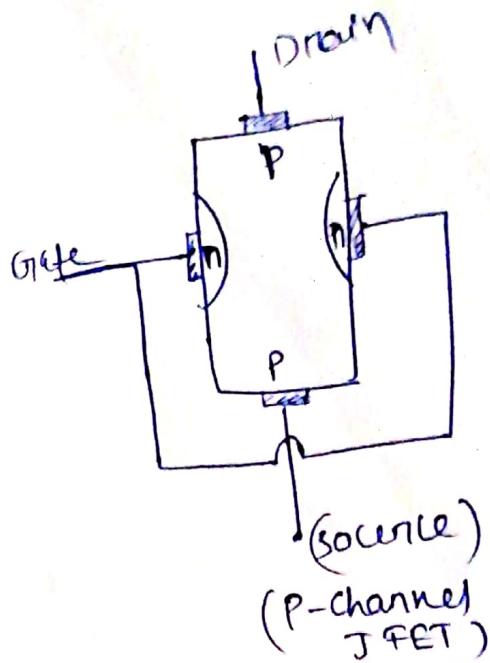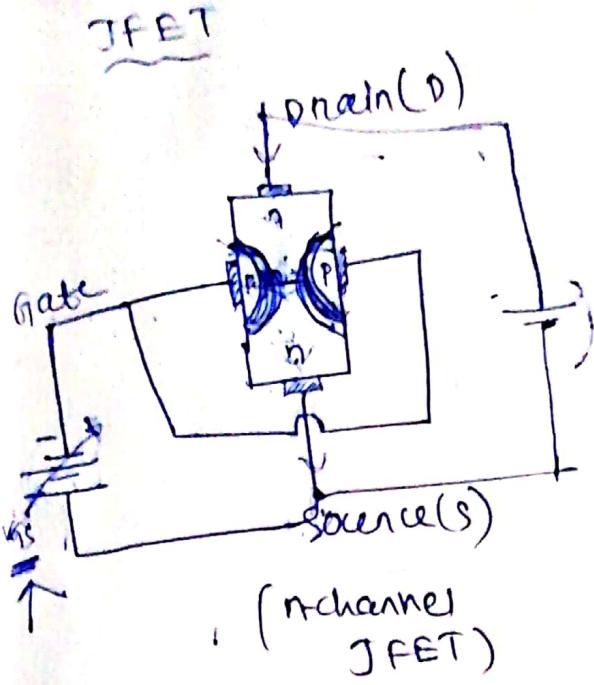
- * stands for Bipolar Junction Transistor
- * Its terminals are emitter, base, collector
- * It is a bipolar device) current flows due to both electron and hole
- * It is a current control device ; the base current controls the collector & current output resistance
- * low input resistance
- * High noisy
- * low efficiency
- * Shorten life
- * low gain band width product



- The voltage between gate and source is such that the gate is reversing biased that the gate and source terminal are interchangeable
- * The voltage between gate and source is such that the gate is reversing biased.
 - * Drain and source terminal are interchangeable
 - * Drain and source resistance/impedance high
 - * $I_g = I_d$
 - ↓
 - source voltage
 - ↓
 - drain current
 - * Two PN junction form two depletion layer
 - * more is the reverse voltage, wider is the depletion layer, narrow the conducting channel and greater the resistance hence source to drain current decreases.

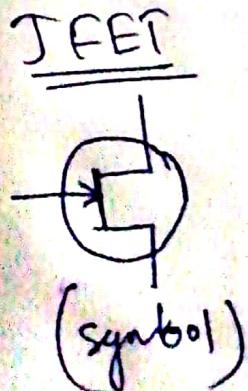

We in bridge oscillator:

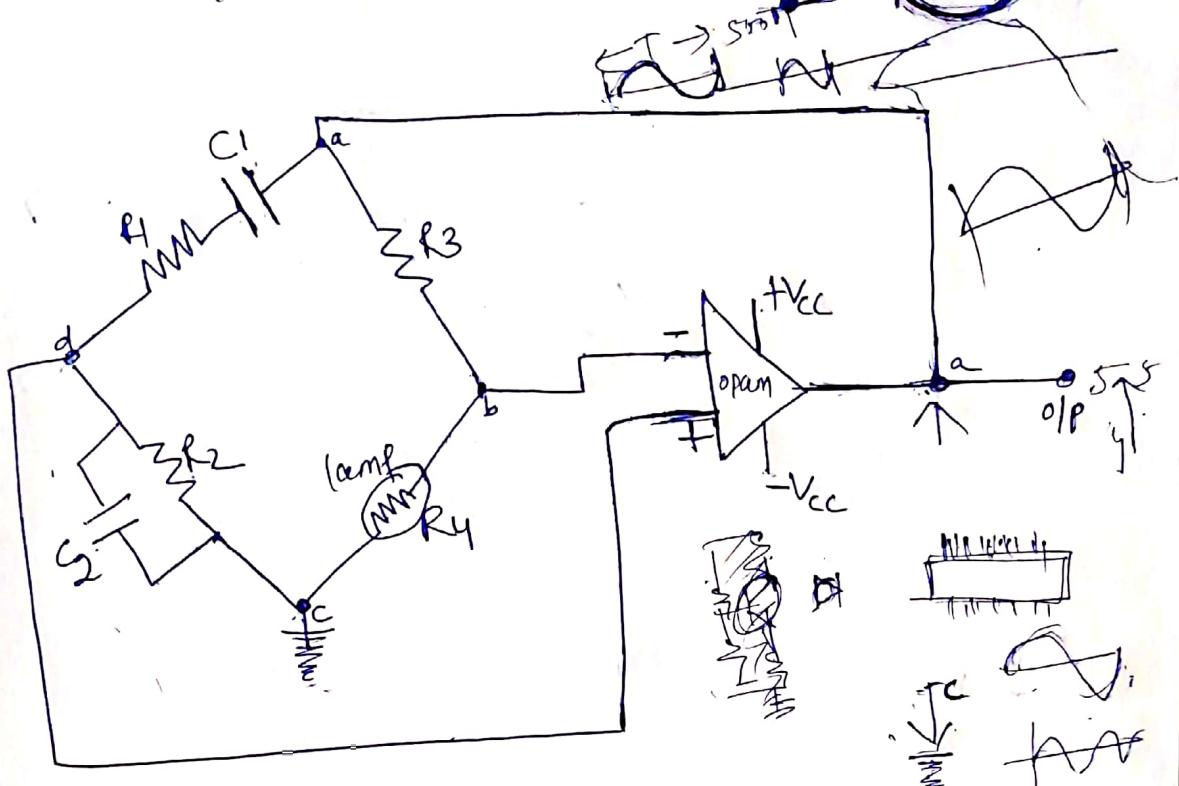

- * It is a audio oscillator .
- * Frequency range of 10Hz to 1MHz can be achieved.
- * R_1, R_2, C_1, C_2 are the frequency adjustment element .
- * op-amp output connected to the bridge point a and c .
- * The bridge circuit output point b and d are input to the op-amp.

~~V.M.~~ The condition for oscillation is :

$$\frac{R_3}{R_4} = \frac{R_1}{R_2} + \frac{C_2}{C_1}$$

~~V.M.~~ The frequency of oscillation is


$$f_0 = \frac{1}{2\pi\sqrt{R_1 C_1 R_2 C_2}}$$

* This oscillator produces constant output if $R_1 = R_2 = R$ and $C_1 = C_2 = C$.

$$f_0 = \frac{1}{2\pi R C}$$


* If output increase or decrease the ramp change and $R_3/R_4 = 2$ [$\because \frac{R_1}{R_2} = \frac{R_1}{R_1} = 1$]

Colpitts oscillator :

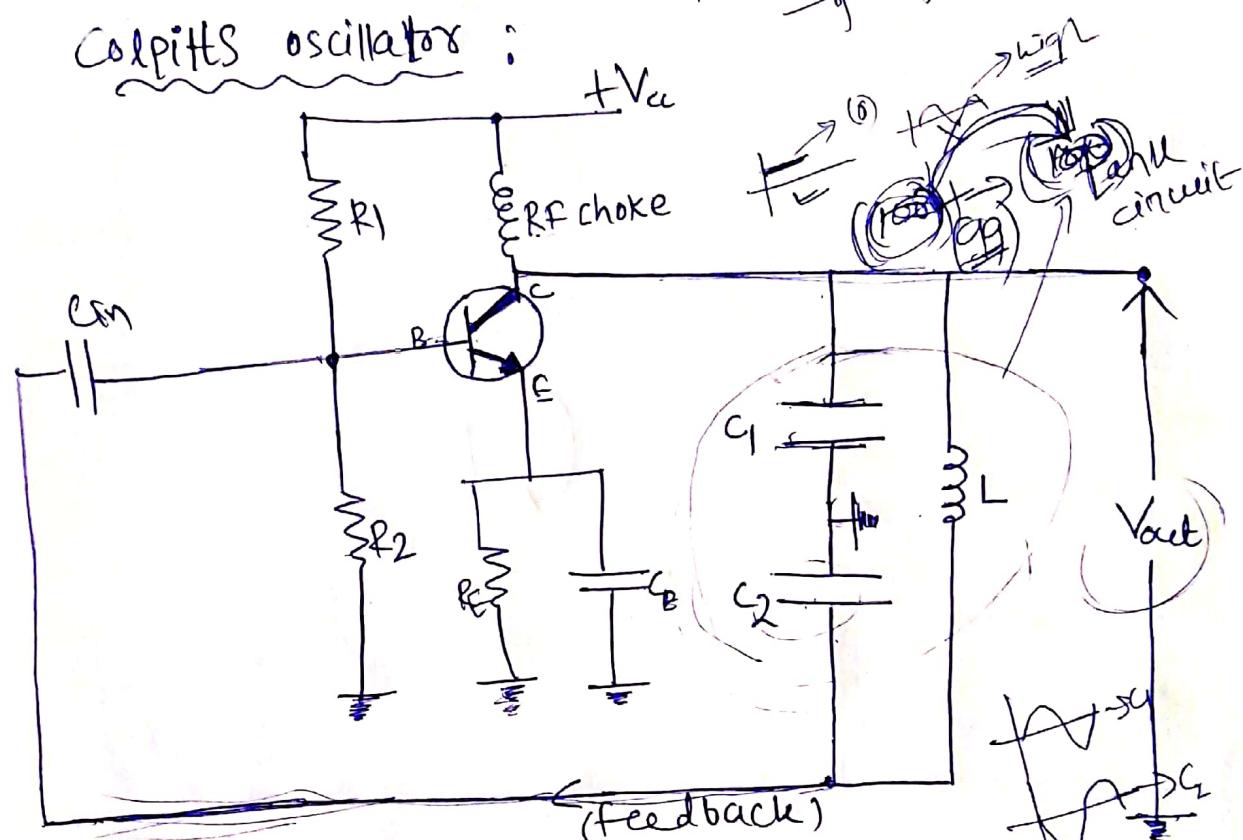

- * Tank circuit is made up of C_1 , C_2 and L .
- * Total capacitance
$$C_{\text{Total}} = \frac{C_1 C_2}{C_1 + C_2}$$
- * C_1 and C_2 charged and discharged through L setting up oscillation
$$f_0 = \frac{1}{2\pi\sqrt{LC_{\text{eq}}}}$$
 $C_{\text{eq}} = C_{\text{Total}}$
- * Output voltage of the amplifier appears across C_1 and feedback voltage developed across C_2 .
- * Voltage across C_2 is 180° out of phase with C_1
- * 180° phase shift by the transistor and further 180° phase shift by ($C_1 - C_2$ voltage divided) which will cause proper undamped oscillation.
- * The choke coil (RF → Radio frequency) allows d.c. to flow and block a.c.


Hartley oscillator

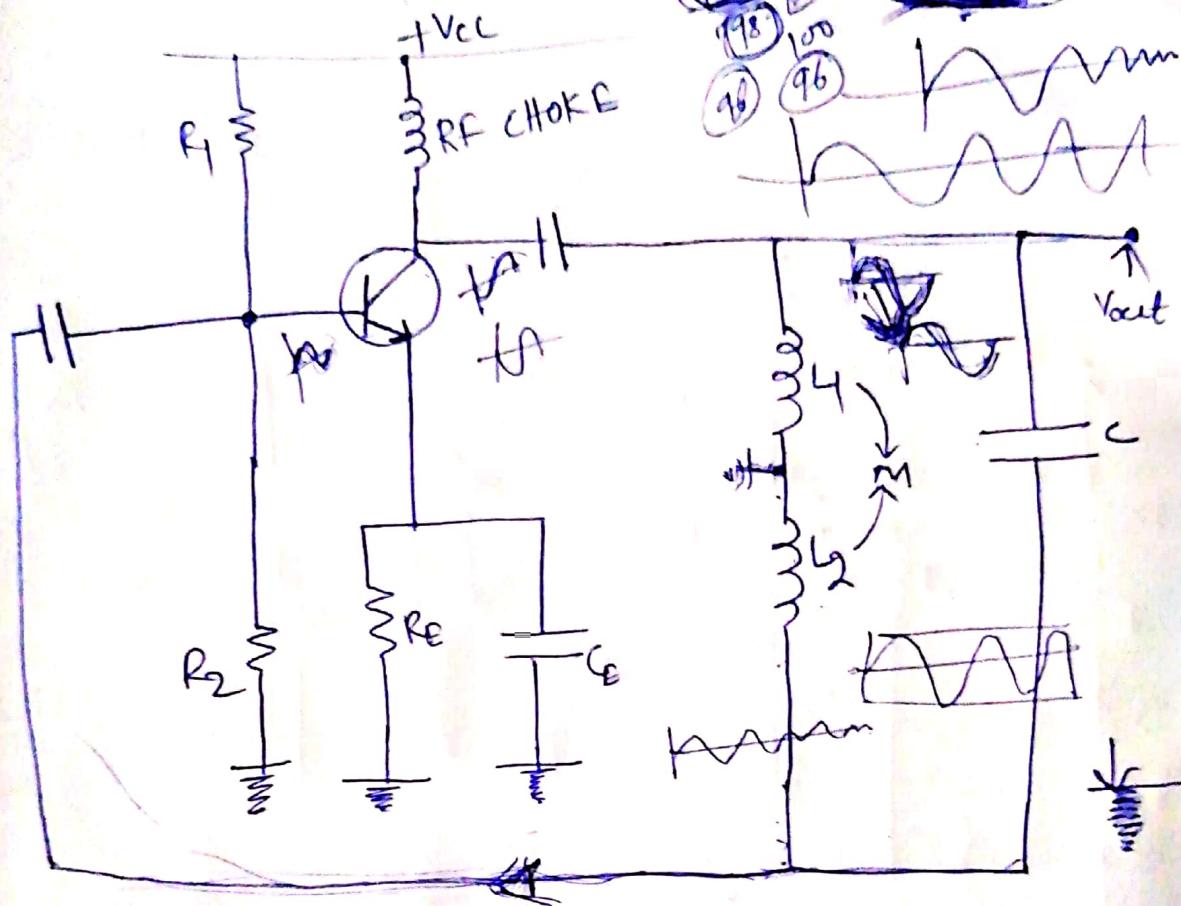

- * It is similar to Colpitt's oscillator with a minor modification, here two inductors are placed in series and a capacitor connected across it. The centre of the inductors tapped across it.
- * The tank circuit is made up of L₁, L₂ and C.
- * The total inductance $L_{\text{Total}} = L_1 + L_2 + 2M$
M = mutual inductance betⁿ L₁ and L₂
- * The frequency of oscillation $f = \frac{1}{2\pi\sqrt{LC}}$
- * When the circuit is turned on the capacitor starts charging, when it fully charges it starts discharging through coils L₁ and L₂.
- * The voltage across L₁ and L₂ are 180° out of phase
- * Transistor provides 180° phase shift and (L₁-L₂ circuit) provides another 180° phase shift.

Phase shift oscillator :=

$$\delta = \frac{1}{2\pi} R C \sqrt{6}$$

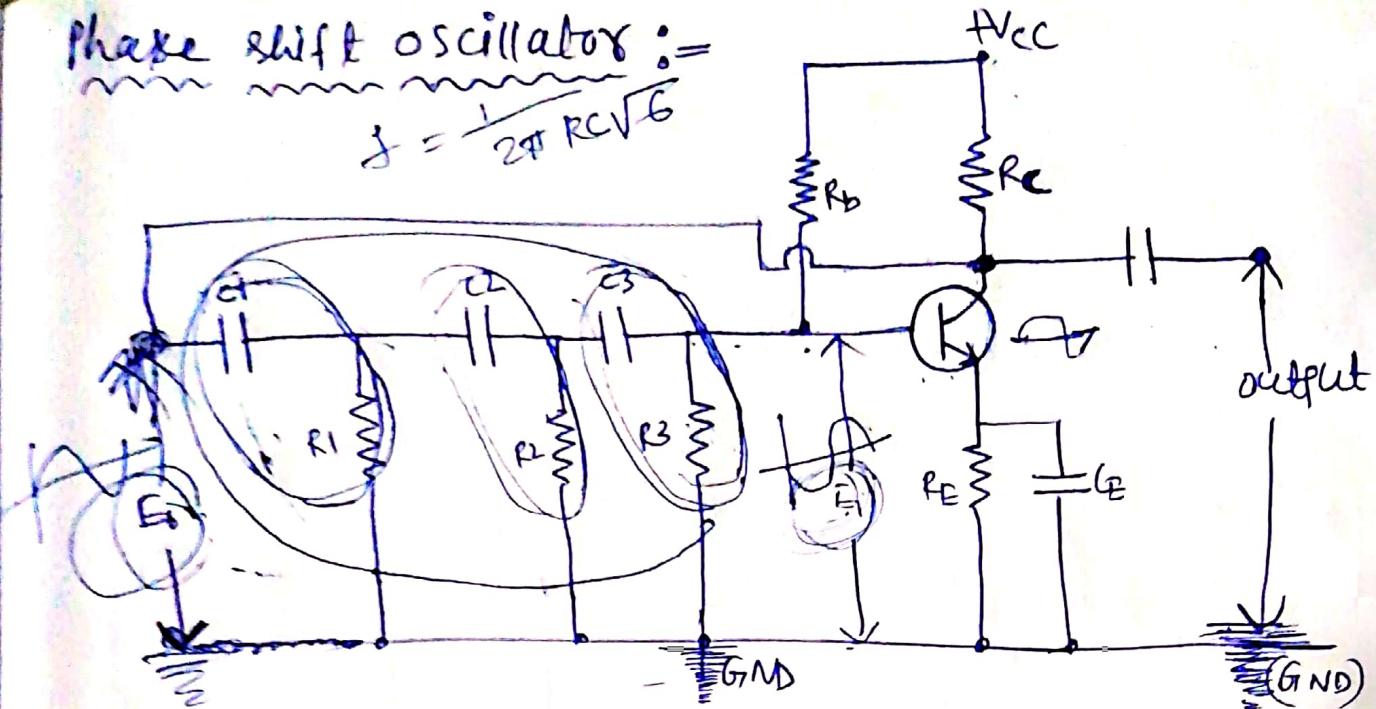

- The phase shift network consist of R_1C_1, R_2C_2, R_3C_3 .
- The phase shift in each RC section is 60° .
the total phase shift produced by the RC network is 180° .
- The frequency of oscillation is given by $f_o = \frac{1}{2\pi R C \sqrt{6}}$

$$\text{for } R_1 = R_2 = R_3 = R \\ C_1 = C_2 = C_3 = C$$

Circuit operation: when the circuit is switched on, it produces oscillation of frequency determined by eqn ①. ~~for~~ 180° phase shift by the (RC) network and a further 180° phase shift by the transistor amplifier.


Advantages:

- ① Not required a transformer or inductor
- ② used to produce very low frequency

Disadvantage:

- i) It is difficult for the circuit to start oscillation as the feedback is small.
- ii) The circuit gives small output.

Tuned collector oscillator:

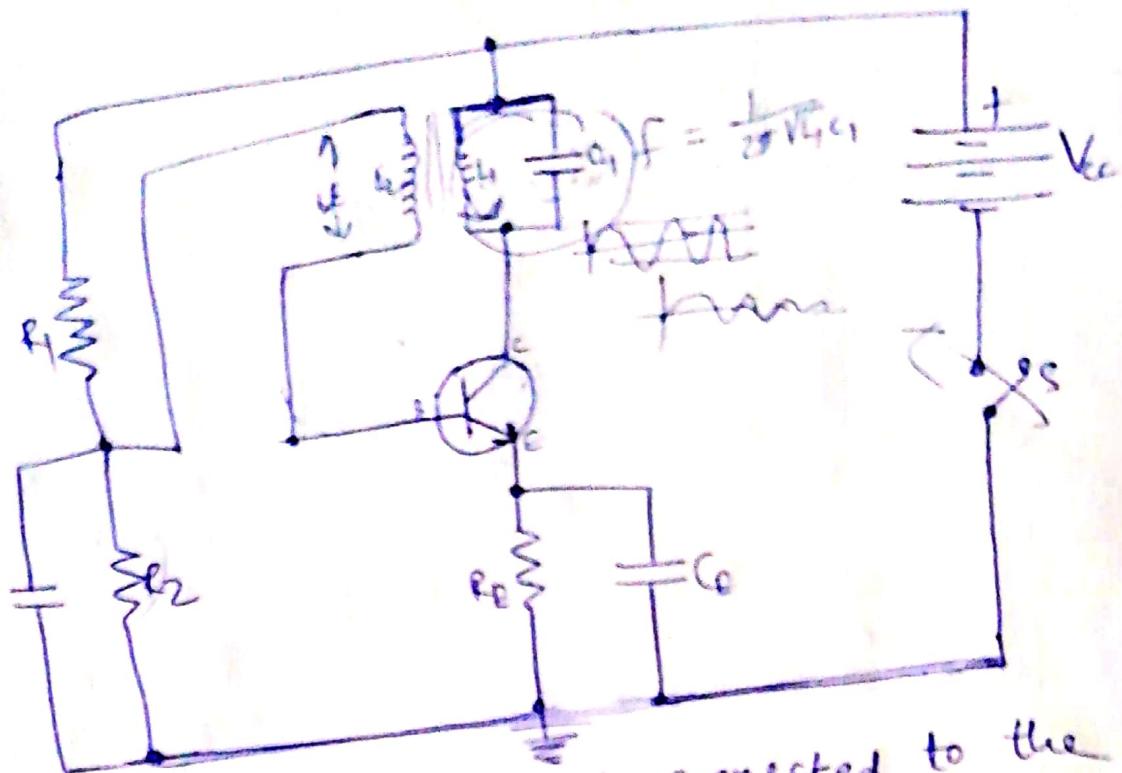

- * The tuned circuit $L_1 C_1$ is connected to the collector.
- * The frequency of oscillation depends on the value of L_1 and C_1 , given by

$$f = \frac{1}{2\pi \sqrt{L_1 C_1}}$$

- * The feedback coil L_2 in the base circuit is magnetically coupled to the primary and secondary coil inductances of a transformer.
- * L_1 and L_2 are basically the potential divider arrangement.
- * The biasing is provided by the potential divider arrangement.

Circuit operation


- > when switch S is closed, collector current starts increasing and charges the capacitor C_1 , when the capacitor is fully charged, it discharge through L_1 , setting up oscillation of frequency $f = \frac{1}{2\pi \sqrt{L_1 C_1}}$.
- > Due to mutual inductance voltage induced in coil L_2 . This voltage get amplified to supply losses to the tank circuit.
- * 180° phase shift achieved by the transformer action.

Parameters of FET

D.C. drain resistance (R_{DS})

static / ohmic resistance

$$R_{DS} = \frac{V_{DS}}{I_D}$$

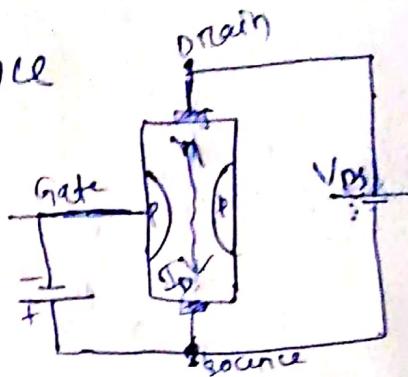

A.C. drain resistance (r_d)

dynamic drain resistance

$$r_d = \left. \frac{\Delta V_{DS}}{\Delta I_D} \right|_{\text{const } V_{GS}}$$

+ It's value ranges from $10k\Omega$ to $1M\Omega$

| If it is the ratio of change in drain to source voltage to change in drain current while V_{GS} constant.

Transconductance / forward transmittance


$$g_m = \left. \frac{\Delta I_D}{\Delta V_{GS}} \right|_{\text{const. } (V_{DS})}$$

(Unit \rightarrow siemens / mho)

Amplification factor (μ)

$$\mu = \left. \frac{\Delta V_{DS}}{\Delta V_{GS}} \right|_{I_D = \text{const}}$$

$$\mu = r_d \times g_m$$

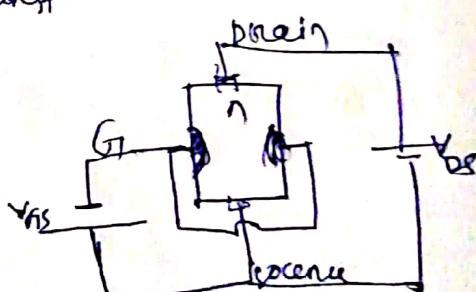

Output resistance (R_o)

$$R_o = \left. \frac{\Delta V_{DS}}{\Delta I_D} \right|_{\text{constant } V_{GS}}$$

It is the ratio of (drain-to-source) voltage V_{DS} to the change in gate-to-source voltage (V_{GS}) at constant drain current I_D .


Biasing of JFET

most commonly used

(a) self bias

(b) potential divider bias

(a) self bias

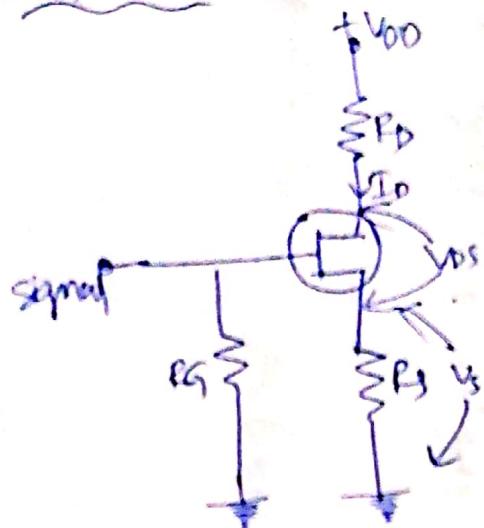


$$V_S = I_D R_S = I_S R_S$$

$$V_{GS} = V_G - V_S$$

$$\boxed{V_{GS} = -I_D R_S}$$

$$\boxed{V_{GS} = -I_S R_S}$$

voltage divider bias

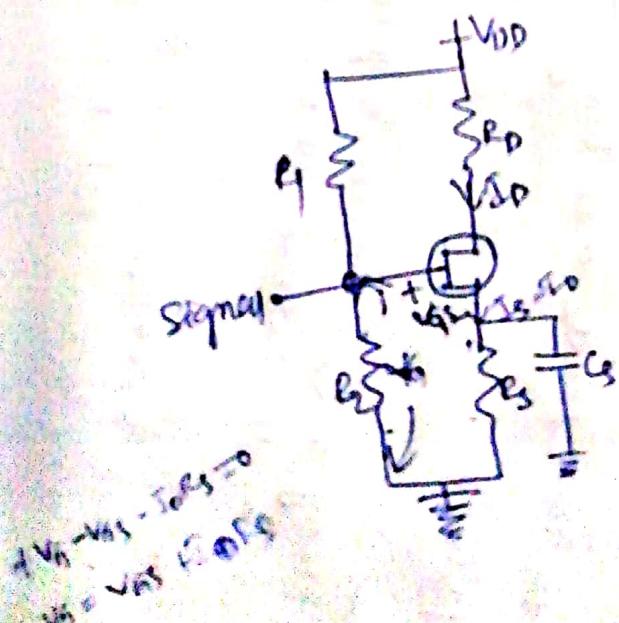

$$\boxed{V_2 = V_G = \frac{V_{DD}}{R_1 + R_2} \times R_2}$$

$$\boxed{V_2 = V_{GS} + I_D R_S}$$

$$\boxed{I_D = \frac{V_2 - V_{GS}}{R_S}}$$

$$\boxed{V_{DS} = V_{DD} - I_D (R_S + R_D)}$$

+ This method provide good stability to operating point.


application of JFET as : (a) as EF amplifier
(b) as a phase-shift oscillator

PUSH-PULL amplifier

Driver section

Output transformer

PUSH-PULL amplifier

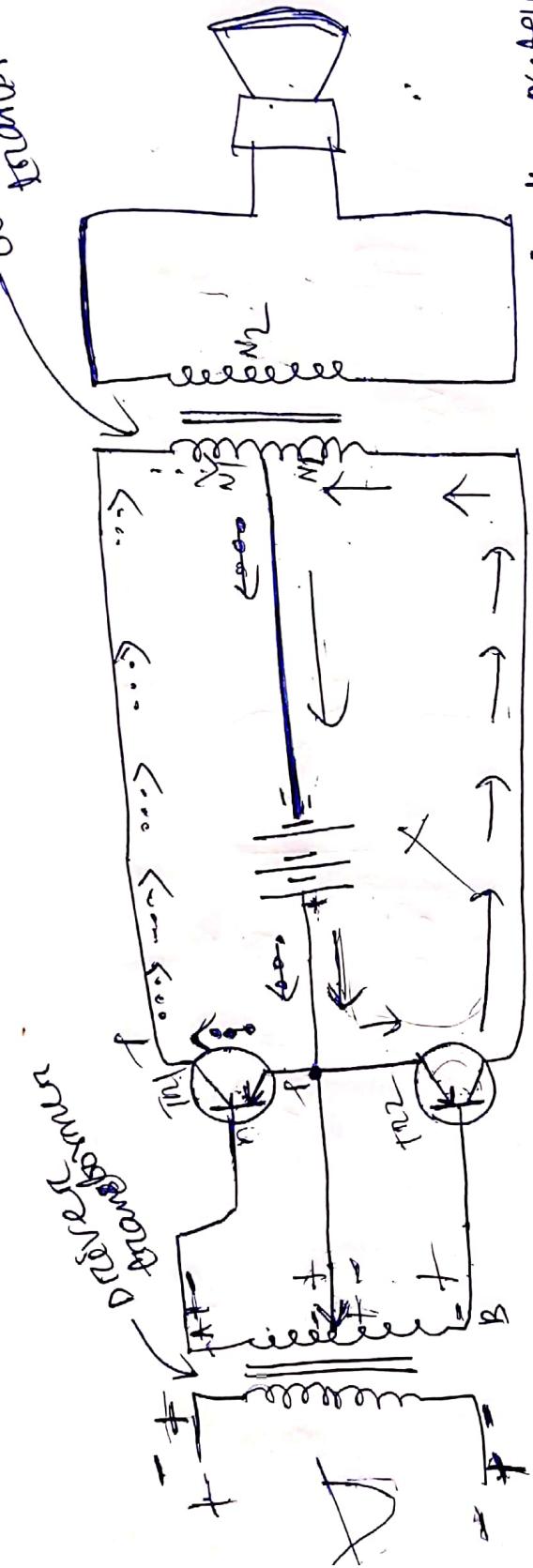

- * Push-pull amplifier is a power amplifier, and is used in the output stages of electronic circuit . It is required whenever high efficiency output power is required .
- * Two transistors are used and operated in class B operation i.e. collector current is nearly zero in the absence of signal .
- * The centre tapped secondary of driver transformer T_1 supplies equal and opposite voltage to the base circuit of two transistors .

Circuit operation:

- * During the first half cycle end A becomes positive and end B becomes negative.
- * This will make the base-emitter junction of T_{R1} reverse biased and that of T_{R2} forward biased. The circuit will conduct current due to T_{R2} only and the T_{R1} forward biased.
- * This will conduct current through T_{R2} and T_{R1} forward bias, hence current path shown by solid line.
- * In the next half cycle T_{R2} reverse biased and the path is shown by dotted line.
- * It allows due to T_{R1} and the path is shown to load through impedance matching, maximum power transfer happens.
- * Efficiency of the circuit is quite high ($= 75\%$) due to class B operation.